

## Examination in MCC015: Superconducting Devices – Fundamentals and Applications

Wednesday May 29<sup>th</sup> 2024, 14.00 – 18.00

Johanneberg SB-L216

Responsible teachers: Alexei Kalaboukhov: 073-7084195, Floriana Lombardi: 031 772 3318

Allowed material: Your choice of calculator and a handwritten A4 page with your own notes.

**You have to answer all problems**

Total credits: **15**:  $\geq 7$  credits passed,  $\geq 10$  credits well passed,  $\geq 13$  credits excellent.

All home assignments and lab reports will be valued and can be used in the evaluation of the exam.

You will get, from all home assignments and lab reports, max **3** credits if exam score is  $< 5$  and max **2** credits if exam score is  $\geq 5$ .

**1. SHORT PROBLEMS (3 credits):**

**1.1** Draw the  $I$ - $V$  characteristic of the Josephson junction for  $Q \ll 1$  (strong damping). By considering the mechanic analog of the junction draw the time dependent voltage across the junction for  $I \approx I_c$  and  $I \gg I_c$ , with  $I_c$  being the critical current of the junction. **(0.5 credit)**

**1.2** Derive the inductance of the Josephson junction as a function of phase difference. **(0.5 credit)**

**1.3** Derive an expression for the Josephson energy for the SNS junction with high transparency where the current-phase relationship is a sum of two components:  $I(\phi) = I_{c1} \sin(\phi) + I_{c2} \sin(2\phi)$  **(0.5 credit)**

**1.4** On what length scale does microwave radiation penetrate a bulk superconductor and how does it depend on frequency? **(0.5 credit)**

**1.5** A dc SQUID with voltage modulation depth of  $\Delta V_{pp} = 40 \mu\text{V}$  is included into the flux-locked loop with negative feedback. The feedback loop resistance is  $R_f = 1 \text{ k}\Omega$  and mutual inductance is  $M_f = 1 \text{ nH}$ . Calculate external magnetic flux that can be applied to produce  $I/8\Phi_0$  in the SQUID loop. Voltage gain of the preamplifier is  $G_{LNA} = 10000$ .


**(0.5 credit)**

**1.6** Describe the detrimental effects on the performance of solid-state-based quantum bits coming from: a. Two-level systems b. Spurious spins **(0.5 credit)**

## 2. RF SQUID (3 credits)

Consider an SNS Josephson junction with a critical current  $I_c = 1 \mu\text{A}$  incorporated in a superconducting ring with inductance  $L = 1 \text{ nH}$  (see Figure 1). An external source supplies a current  $I$ , a part of which ( $I_L$ ) passes through the ring and a part ( $I_J$ ) through the junction. Calculate the value of the total current  $I$  supplied by the source if the current through the junction  $I_J$  is equal to  $I_c$ .

Figure 1

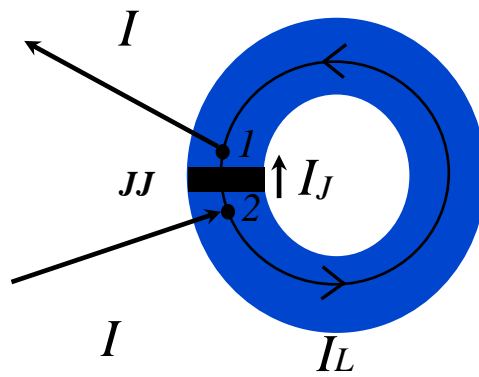

### 3. RSJ model of the Josephson junction (3 credits)

**3.1** A small area Josephson junction is biased with a constant current  $I_B$  which is much less than the critical current  $I_C$  in the period of time  $-\infty < t \leq 0$ . At  $t = 0$  the bias current is reduced to 0. Consider you can model the junction with an RSCJ circuit and that you can linearize the differential equation describing the junction behavior assuming  $I_B \ll I_C$ . Derive the dynamic of the junction  $\varphi(t)$  at  $t \geq 0$  in the case of a small capacitance  $Q \ll 1$ . **(1.5 credits)**

**3.2** Consider a constant voltage source  $V_0$  connected across the Josephson junction. Using the RCSJ model, find the total current through the junction  $I_{TOT} = I_C + I_J + I_R$  averaged over one time period  $\Phi_0/V_0$ . Plot the I-V characteristic of such voltage biased junction. Does it depend on the quality factor of the Josephson junction? Motivate your answer. **(1.5 credits)**

**4. Free energy of the rf SQUID (3 credits)**

The total free energy of the superconducting loop with one Josephson junction (rf-SQUID) consists of two contributions from the Josephson and magnetic energy parts. Derive the total free energy of the rf SQUID in the absence of externally applied magnetic flux as a function of total current in the loop and make a schematic plot of this dependence. Show that for  $\beta_{L,rf} < 1$  there is only one local minima at zero current. How many local minima corresponding to metastable energy states are at  $\beta_{L,rf} = 30$ ?

**5. Microwave properties of superconductors (3 credits)**

Consider the superconducting half wave coplanar wave guide resonator of length  $d$  depicted in Fig. 2(a) connected at the two ends to transmission lines of impedance 50 Ohm via the coupling capacitors  $C_1$  and  $C_2$ .

The input impedance of a transmission line terminated with a load  $Z_L$  at a distance  $d$  is given by

$$Z_{TL} = Z_0 \frac{Z_L + Z_0 \tanh \gamma d}{Z_0 + Z_L \tanh \gamma d},$$

with the characteristic wave impedance for small losses  $Z_0 \approx \sqrt{\frac{L_l}{C_l}}$ , with  $L_l$  and  $C_l$  the inductance and capacitance per unit length of the transmission line.

For an open-circuited transmission line resonator  $Z_L \rightarrow \infty$  the above expression simplifies to

$$Z_{TL} = Z_0 \coth \gamma d$$

The wave propagation constant is given by  $\gamma = \alpha + i\beta$ , where  $\alpha$  is the attenuation constant and the phase constant for small losses can be written as  $\beta \approx \omega \sqrt{L_l C_l}$ , with  $\omega$  the angular frequency.

- 1) Which material parameters of the superconductor enter the attenuation constant  $\alpha$  and phase constant  $\beta$ ? **(0.5 credits)**
- 2) What is the value of the product of the phase constant and the length of the half-wave resonator,  $\beta d$ , at the resonance condition  $\omega = \omega_r$  of the lowest fundamental mode? Illustrate your answer by sketching the voltage along the transmission line. **(0.5 credits)**
- 3) Close to the resonance frequency  $\omega = \omega_r + \Delta\omega$  we can write for the input impedance of the half wave resonator:

$$Z_{TL} = \frac{Z_0}{\alpha d + i \frac{\pi \Delta\omega}{\omega_r}} = \frac{Z_0}{\alpha d + i \Delta\omega \sqrt{L_l C_l}}$$

The equivalent lumped element LCR circuit show in Fig. 2b close to resonance frequency  $\omega = \omega_0 + \Delta\omega = \frac{1}{\sqrt{LC}} + \Delta\omega$  given by

$$Z_{LCR} = \frac{R}{1 + 2iRC\Delta\omega}$$

Mapping those two impedance expressions find the expressions of the equivalent resistor, R, capacitor C, and inductance L. **(2 credits)**

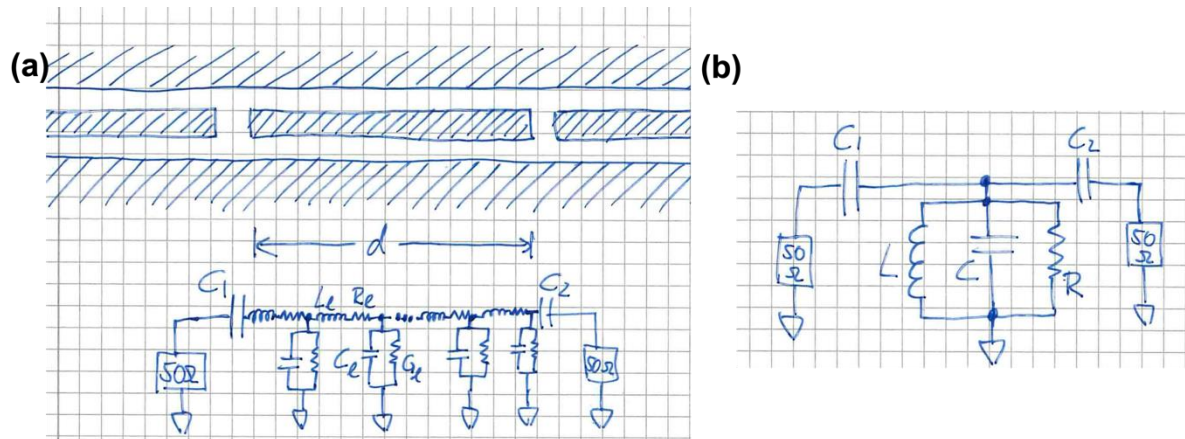


Figure 2. (a) The top panel is a top view of a coplanar waveguide half-wave resonator with the hatched regions being the superconducting film. The bottom panel is the equivalent transmission line circuit. (b) Equivalent lumped element circuit of the half-wave resonator close to resonance frequency.